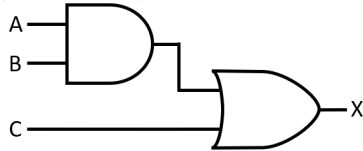


This worksheet is about getting familiar with logic gates and circuits.


□ Task 4 Solution.1

- Draw the following circuit diagrams (note there are different notations!): **In these diagrams I have used X to denote the output.**


1. $(A \text{ AND } B) \text{ OR } C$




2. $AB + C$

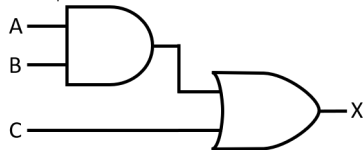


3. $(A + BC) + D'$

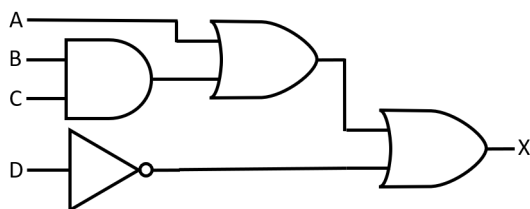

4. $(A \text{ XOR } B) \text{ NAND } C$

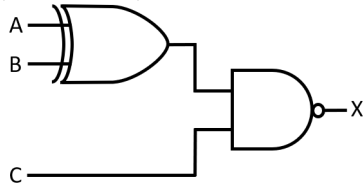

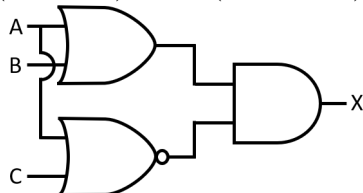5. $(A \text{ OR } B) \text{ AND } (C \text{ NOR } A)$



□ Task 4 Solution.2

- Write the truth table for each of the above expressions.

1.

$(A \text{ AND } B) \text{ OR } C$			
A	B	C	Output
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

2.

$AB + C$			
A	B	C	Output
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

3.

$(A + BC) + D'$				
A	B	C	D	Output
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1


4.

$(A \text{ XOR } B) \text{ NAND } C$			
A	B	C	Output
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1


5.

$(A \text{ OR } B) \text{ AND } (C \text{ NOR } A)$			
A	B	C	Output
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0


□ Task 4 Solution.3

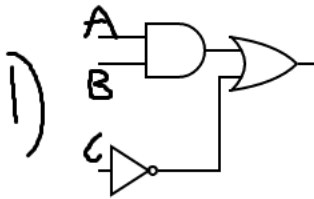

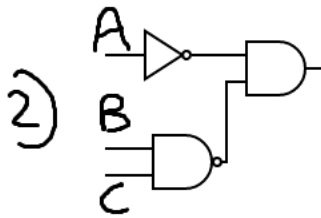- 1:
- A AND B OR NOT C
 - $A \cdot B + C'$
 - $AB + \neg C$



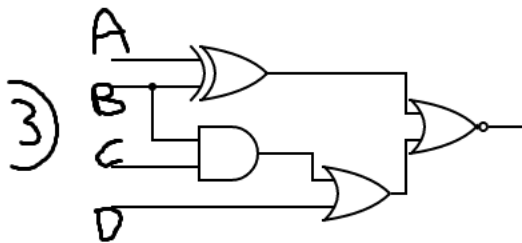- 2:
- NOT A AND (B NAND C)
 - $A' \cdot (B \cdot C)'$
 - $\neg A \neg (BC)$



- 3:
- (A XOR B) NOR ((B AND C) OR D)
 - $((A \oplus B) + (B \cdot C + D))'$
 - $\neg((A \oplus B) + (BC + D))$