

This worksheet is about getting familiar with logic gates and circuits.

### □ Task 4.1

- Draw the following circuit diagrams (note there are different notations!):
  1.  $(A \text{ AND } B) \text{ OR } C$
  2.  $AB + C$
  3.  $(A + BC) + D'$
  4.  $(A \text{ XOR } B) \text{ NAND } C$
  5.  $(A \text{ OR } B) \text{ AND } (C \text{ NOR } A)$

### □ Task 4.2

- Write the truth table for each of the above expressions.

### □ Task 4.3

- Give the boolean expressions for each of the following:

